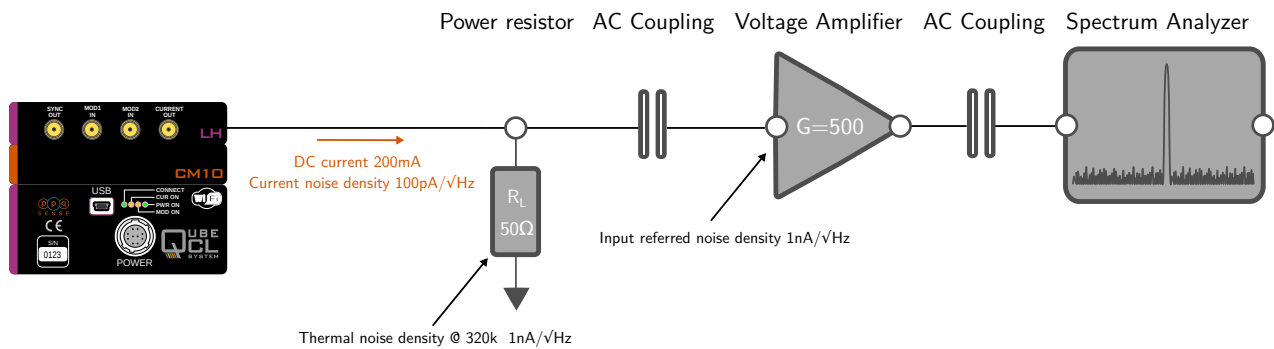


# 1 QubeCL Noise Measurement Setup

## 1.1 introduction

The QubeCL current noise is so low that it needs a specific setup to be measured. The goal is to be able to measure noise spectral densities on the order of  $100\text{pA}/\sqrt{\text{Hz}}$ , to do this we must use an amplification stage that does not degrade the quality of the input signal, for this purpose the following measurement setup was used.



**Figure 1:** Current noise measurement setup

A current of  $200\text{mA}$  is supplied to a  $50\Omega$  resistor, and noise is AC-coupled to a voltage amplifier with gain  $G = 500$ . The thermal noise of the resistor and the input noise of the amplifier stage do not substantially degrade the measurement. The current noise is amplified for a total transimpedance gain of 25000 given by  $G \cdot R_L$  without appreciable alteration, so it can be easily measured with a common spectrum analyzer.

## 1.2 Current Noise Power Spectral Density (CNPSD) calculation

Typically the measurement taken on a spectrum analyzer is given in dBm units, to switch to  $\text{nA}/\sqrt{\text{Hz}}$  representation the following relationships are used:

The noise power expressed in dBm is defined as:

$$P_{noise}[\text{dBm}] = 10 \cdot \log\left(\frac{V_{noise}^2}{50\Omega} \cdot 1000 \cdot RBW\right)$$

$V_{noise}$  is the noise level at the input of the spectrum analyzer expressed in Volts,  $RBW$  is the resolution bandwidth of the measurement expressed in  $\text{Hz}$ .

The expression of  $V_{noise}$  is:

$$V_{noise} = \frac{I_{noise}}{10^9} \cdot G \cdot R_L$$

$I_{noise}$  is the current noise expressed in  $\text{nA}$ ,  $G$  is the gain of the voltage amplifier,  $R_L$  the value of the load resistor expressed in  $\Omega$ .

Using these relationships, we obtain the expression of current noise spectral density expressed in  $nA/\sqrt{Hz}$  as:

$$I_{noise}[\frac{nA}{\sqrt{Hz}}] = (10^{\frac{P_{noise}}{10}} \cdot \frac{1}{RBW} \cdot \frac{50}{1000})^{\frac{1}{2}} \cdot \frac{1}{G \cdot R_L} \cdot 10^9$$

$P_{noise}$  is the Power noise expressed in dBm.

This relationship is used to obtain the spectral noise density plot presented in the QubeCL datasheet from measurements taken with the spectrum analyzer.

### 1.3 Final consideration

In order to obtain a good noise measurement, it is necessary for all components of the setup to be wired properly. Shielding and good dissipation of load resistance  $R_L$  is recommended. The power supply for the entire system must be highly filtered; batteries can also be used as an alternative.